

用實測教導模型歸納與分析 —以訊號之反射實驗為例

林志民

中央研究院原子與分子科學研究所

國立臺灣大學化學系

1

如果小的時候只會考試，我怕
老了連試都考不好



2

相當多的研究是無法預知結果的，而是從現有的實驗結果，做分析與歸納，找出規律，進而建立物理模型，再而能預測類似實驗的結果或做出新穎的設計。

個人發現，學生普遍欠缺此類經驗。學生的物理模型，多由書本或教師告知而來；學生研究工作中的預測或設計，常由老師代勞。畢竟，此類工作極依賴經驗(沒有人生下來就有經驗)，大部分的學生無法立即進行上述完整的研究流程。

為此，本人設計了一套題目，要求學生在一週內，由自己的實驗結果建立模型，並互相驗證，優者可試著做出新設計。有趣的是，在此練習中，愈年輕的學生反應愈好。

3

My Goal is

*To Simulate a Research Process
with Real Experiments.*

There is no substitution for experiments.

4

A Research Process:

To measure something new

To describe and explain the measurements


(科學家 *or* 記者)

To build a model

To test the model by more experiments

To predict new things with the model

5

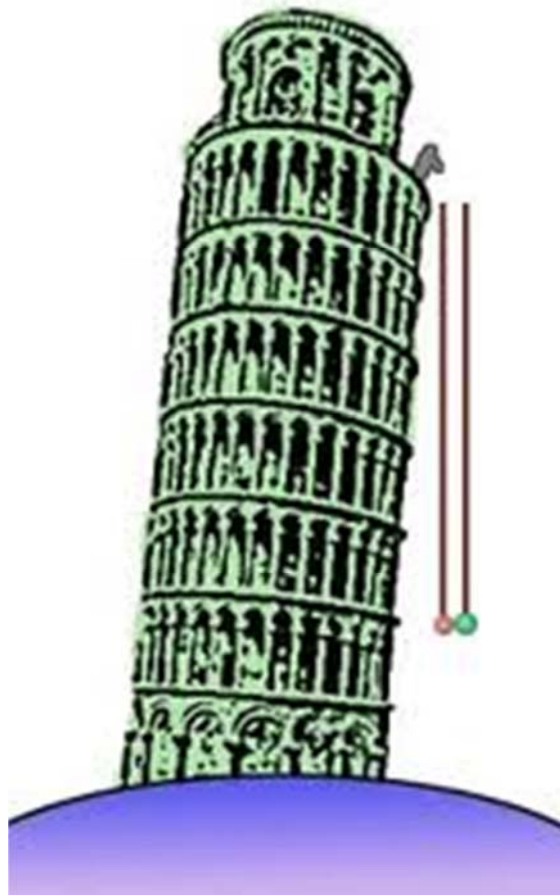

6

Why Simulation?

Faster	< 1 week
Lower cost	< 10,000 NTD
More exact	< 10% error

7

Why 訊號之反射實驗?

When I was young, ...

It is not easy to find the answer on Web.

Difficult enough ...

yet easy enough ...

It happens everyday.

8

只給實驗目標、不給步驟

要求學生自行決定測量範圍

逐日檢查實驗結果：

- 1) 避免錯得太遠 (小錯是好的)
- 2) 確定達到該有的精確度
- 3) 協助養成良好的實驗習慣

9

For example: (after a simple demo experiment)

Mission 1:

(1a) Measure the speed of an electric pulse propagating in a coaxial cable.

(1b) Measure the voltage reflection coefficient of a 50Ω coaxial cable which is terminated with: (i) resistive loads; (ii) capacitive loads; (iii) inductive loads.


You should choose a suitable range of resistors, capacitors and inductors and a suitable frequency range (pulse width) to make the measurements **meaningful**.

(1c) Make a R+C load that matches a 50Ω coaxial cable for fast pulses (width ≤ 100 ns) but has almost zero current for dc voltage (≥ 1 us). Also check pulses of very large widths.


(1d) Make a short pulse generator, of which the pulse width is controlled by the cable length. A fast high voltage switch is provided. [Do (1d) after all other training missions].

10


(Long) Coaxial Cable ($Z_0 = 50 \Omega$)

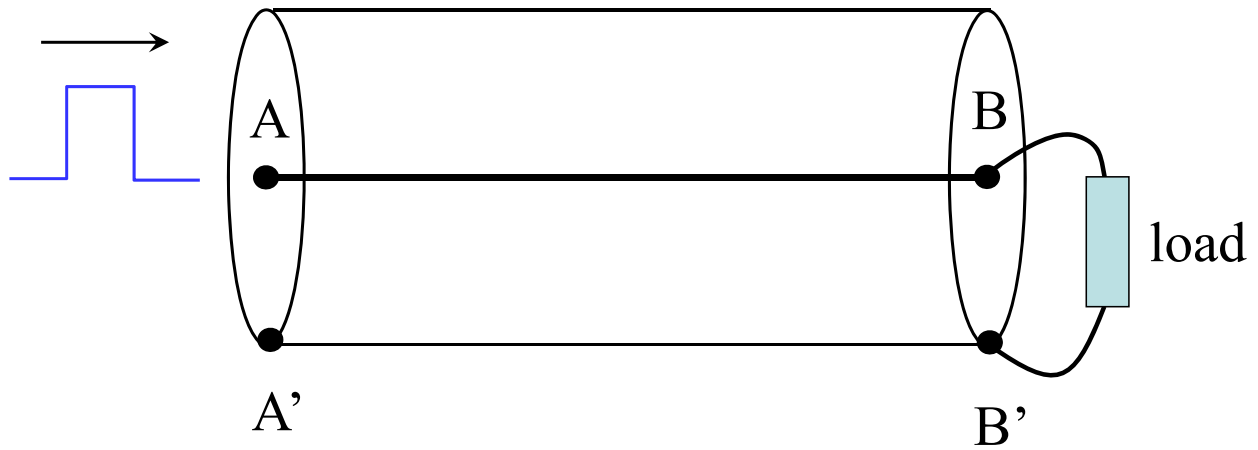

To Monitor: Waveforms at A/A' and B/B'

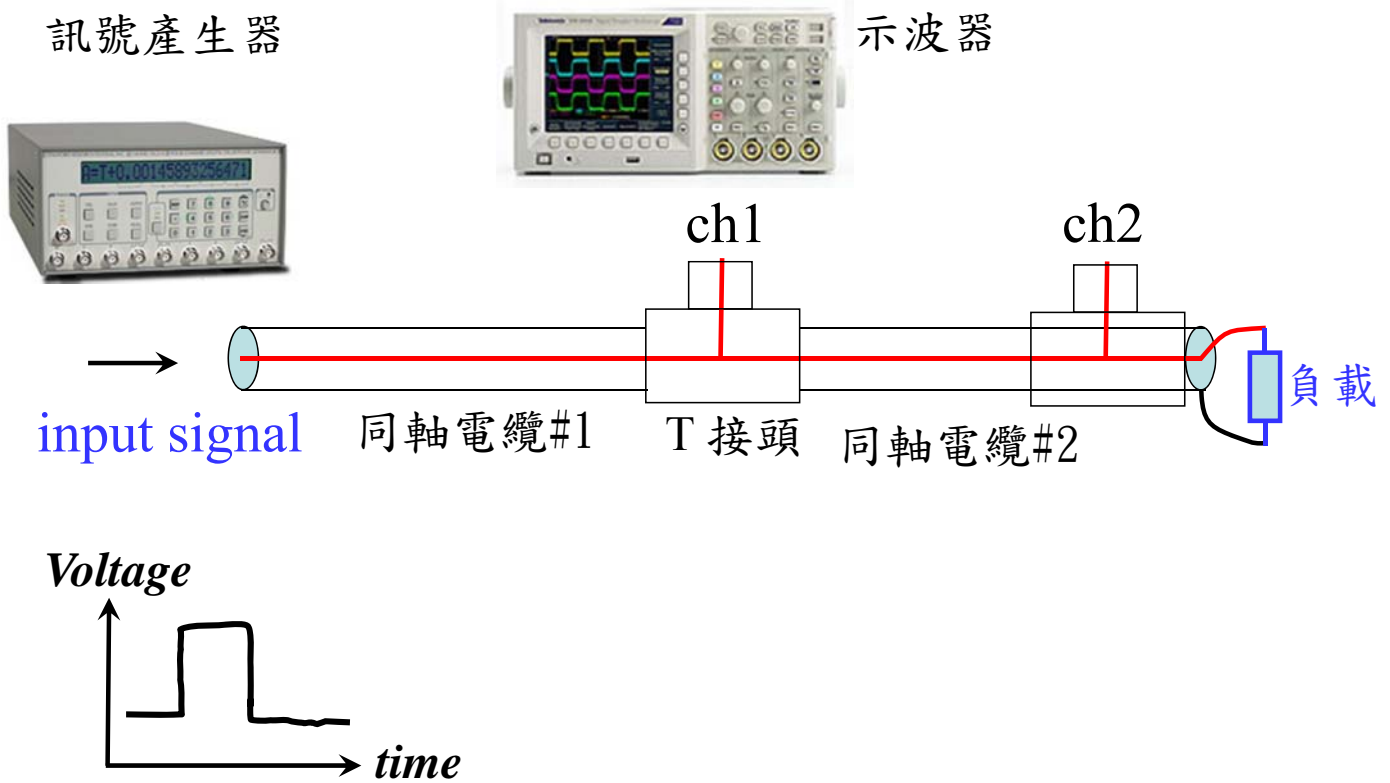


Only cable #1

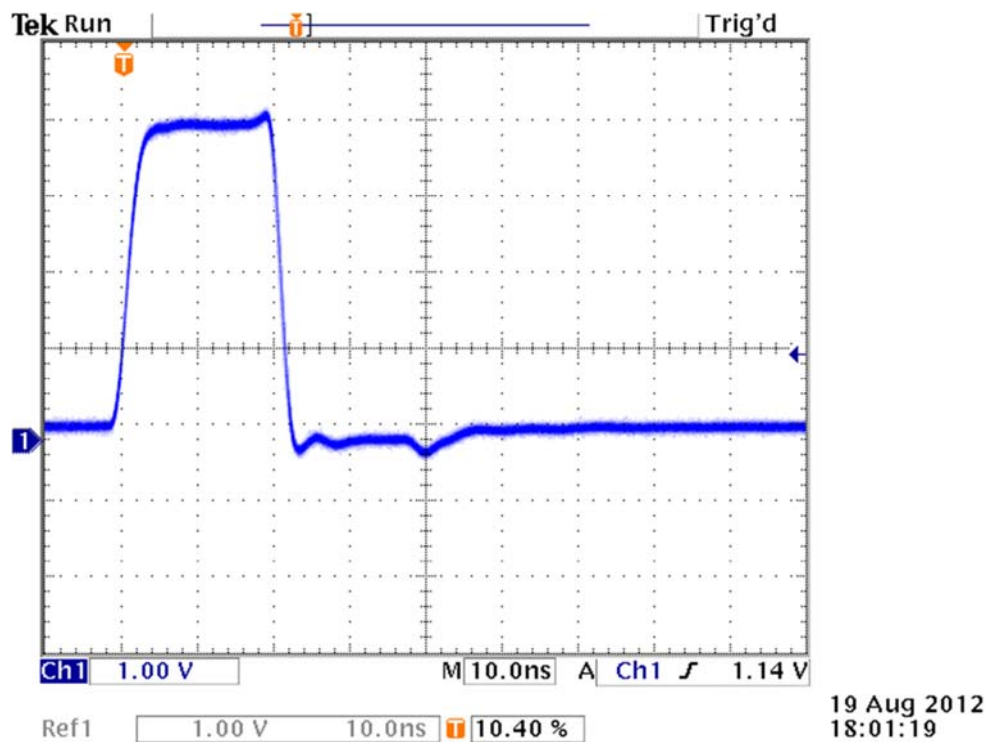

13



cable #1 and cable #2

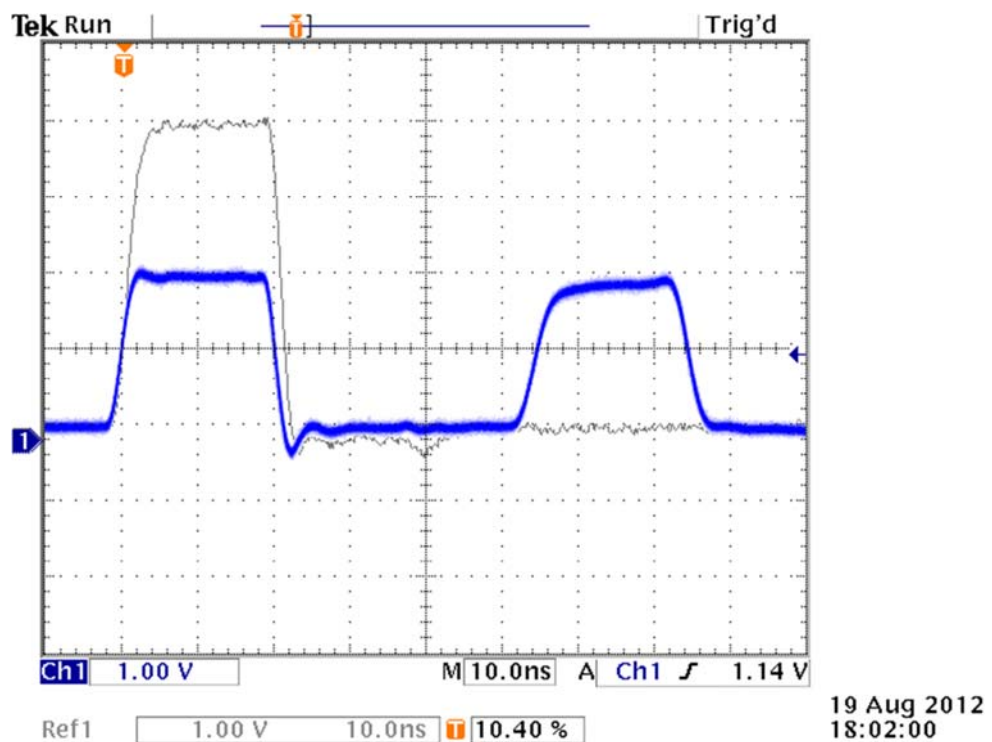

Not only surprise. We require the student to perform analysis


14

Load = open ($\infty \Omega$)

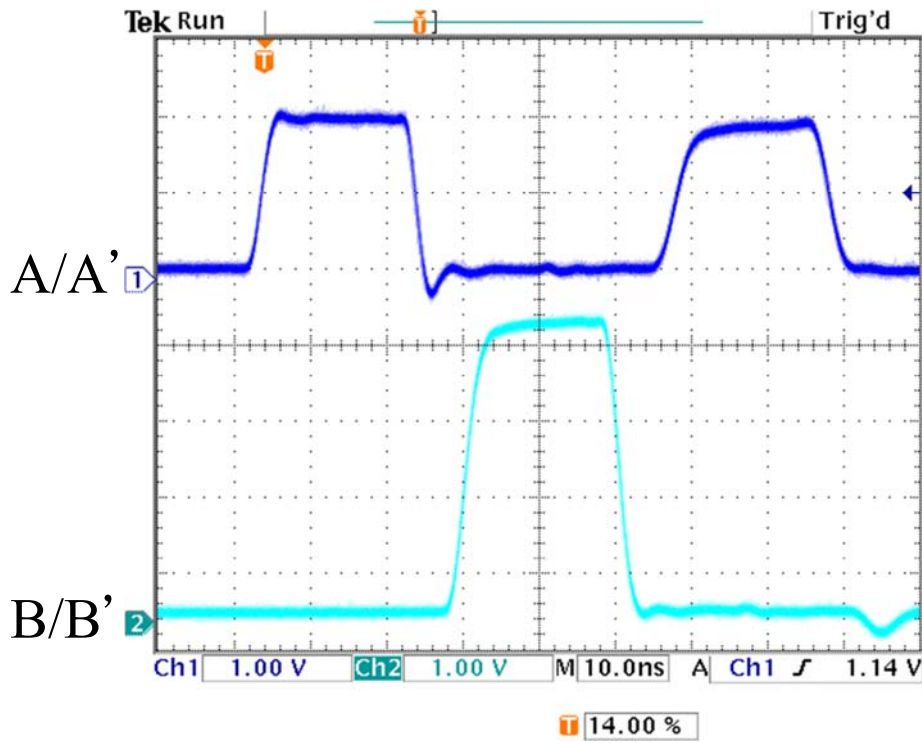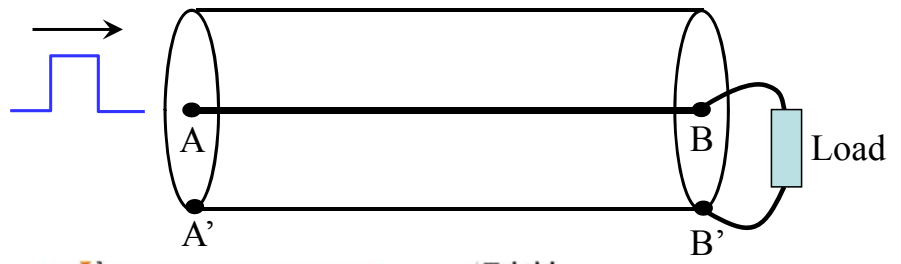

19 Aug 2012
17:42:16


Load = 50Ω (impedance matched)

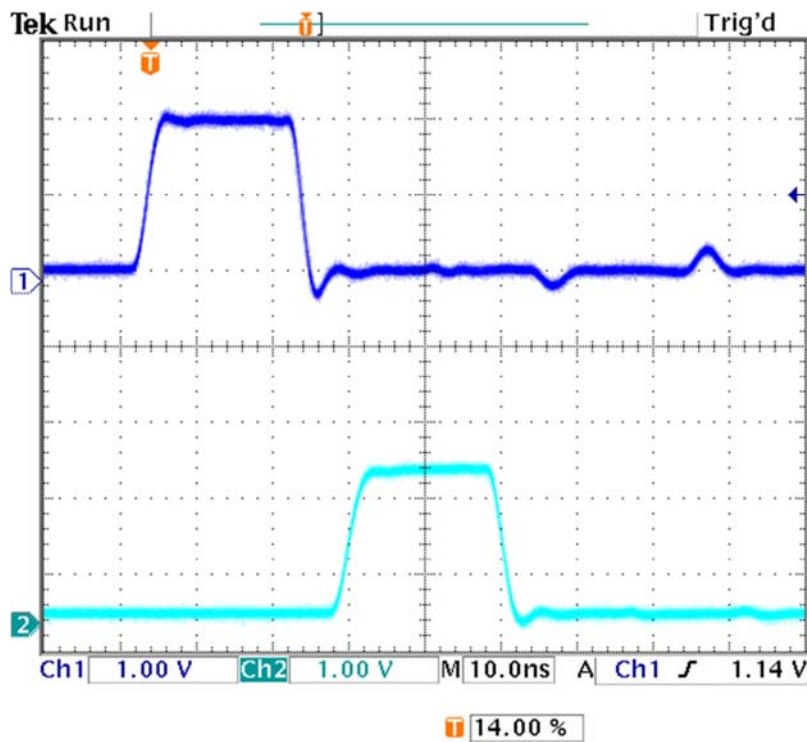

19 Aug 2012
17:36:19

Delay is due to the length of the cable

Load = short (0Ω)

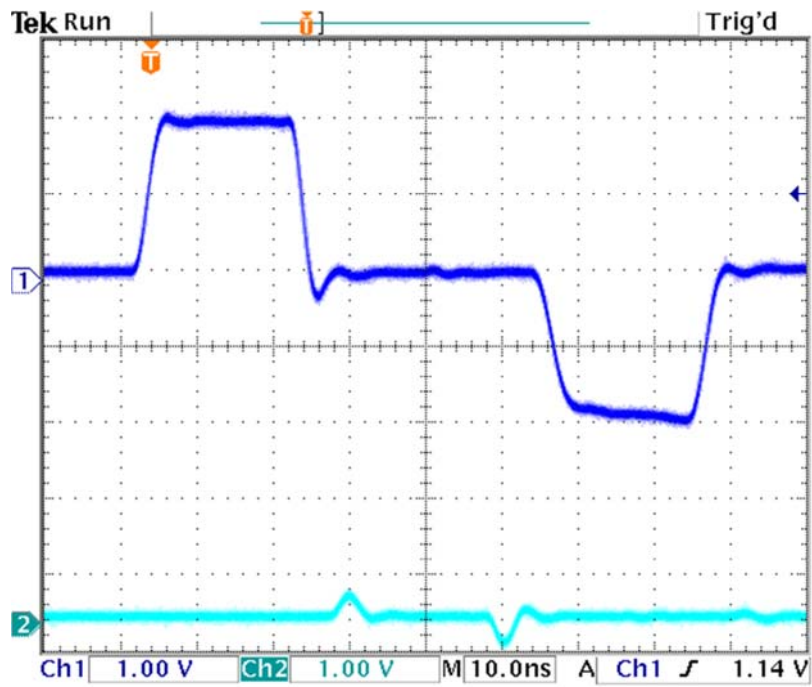


19 Aug 2012
17:44:52

14.00 %

17

Load = 172Ω

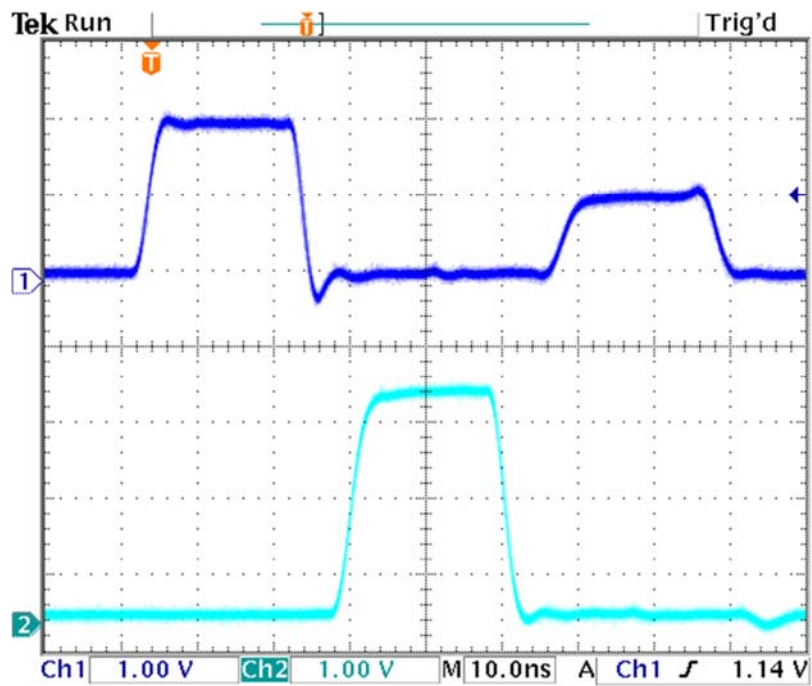


19 Aug 2012
17:46:17

14.00 %

18

Load = 15 Ω

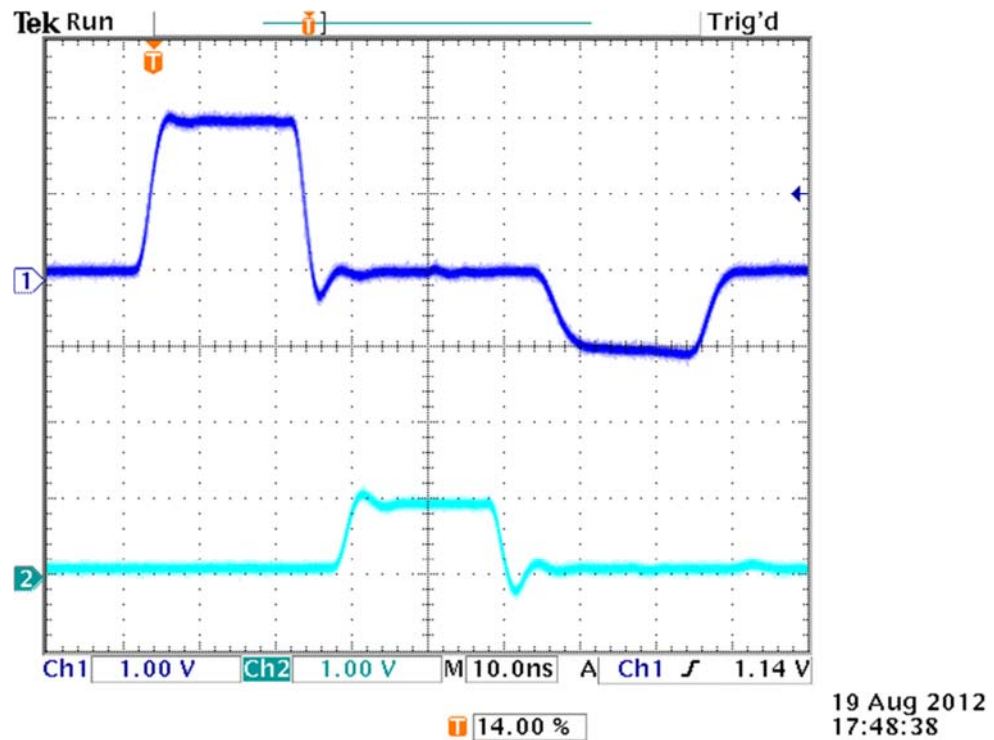

19

Essential Concepts:


1. Length matters at short time scales.

Length of a coaxial cable causes time delay.

For non-coaxial cable, using very short wires to approximate the ideal case.

20



Load = copper wires **15 cm Vs. 1 cm**

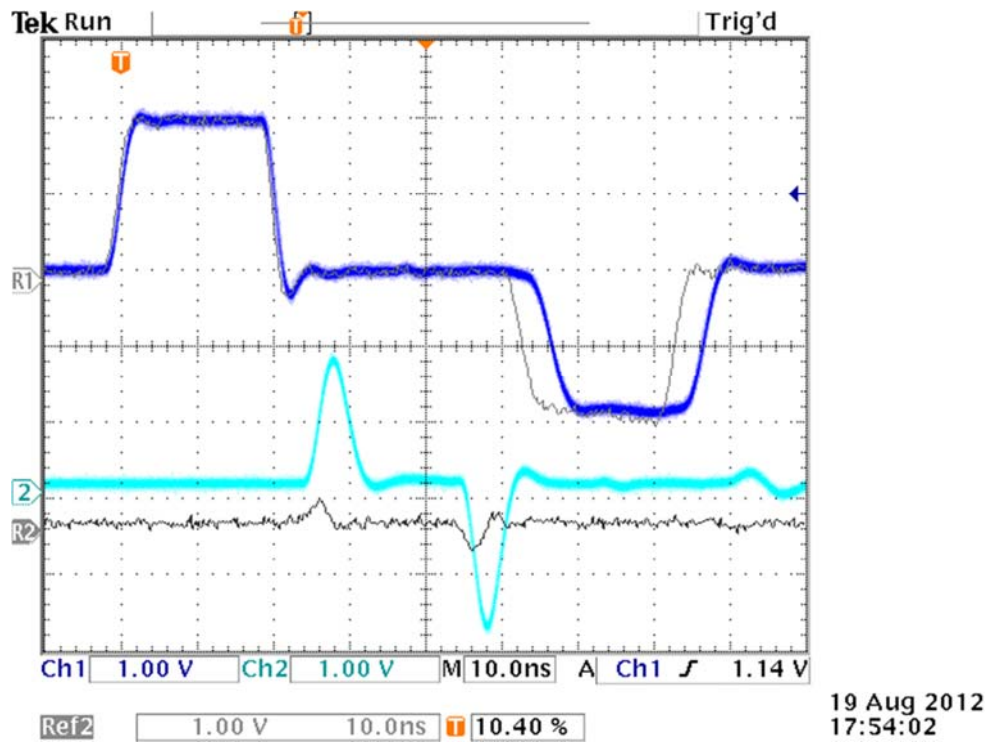

21


Essential Concepts:

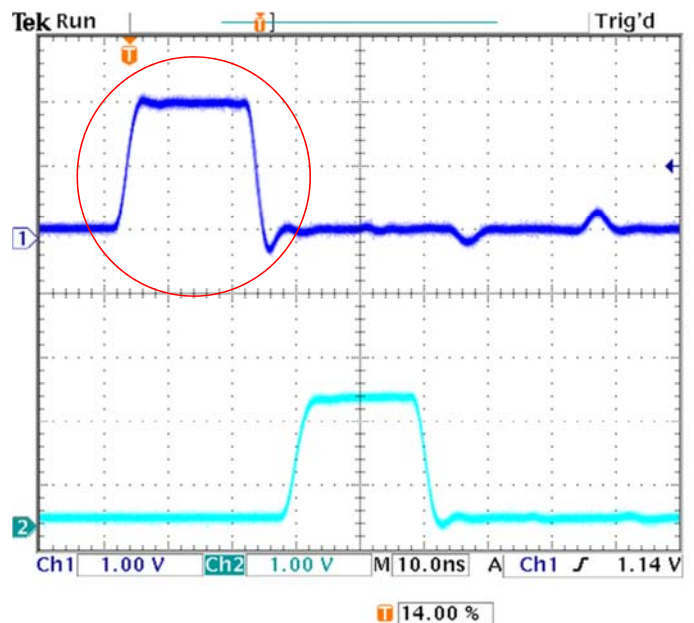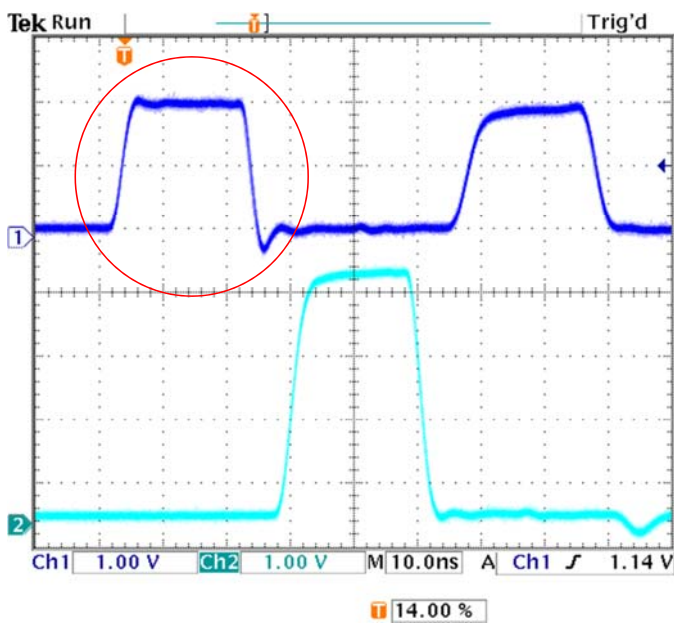2. What happens before the signal reaching the cable end?



22

Clues:

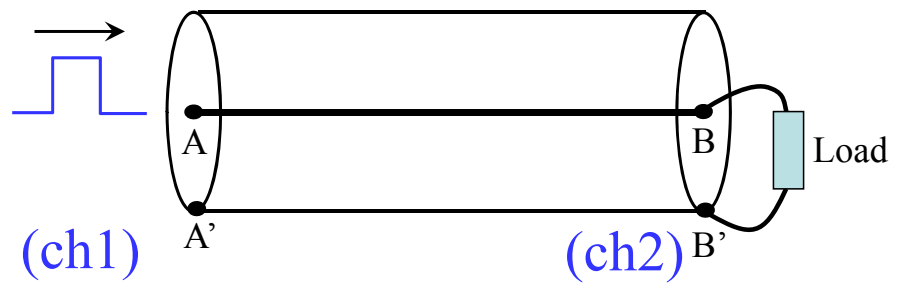


1. Signal propagation speed can be measured. $\cong \frac{2m}{10ns}$
2. The reflected signal can be monitored at A/A' if the coaxial cable is long enough.
3. The load voltage can be measured at B/B'.
4. The impedance concept of a coaxial cable can be verified by using a matched termination.

23

Essential Concepts:

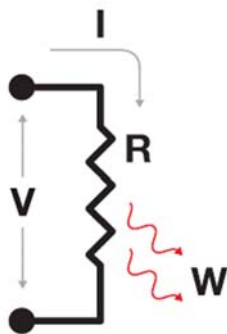1. Length matters at short time scales.
2. What happens before the signal reaching the cable end?
3. Apply the Ohm's Law carefully.




Voltage Drop $\Delta V = iR$

Not V

24

$$i_{in} = i_L + i_R$$

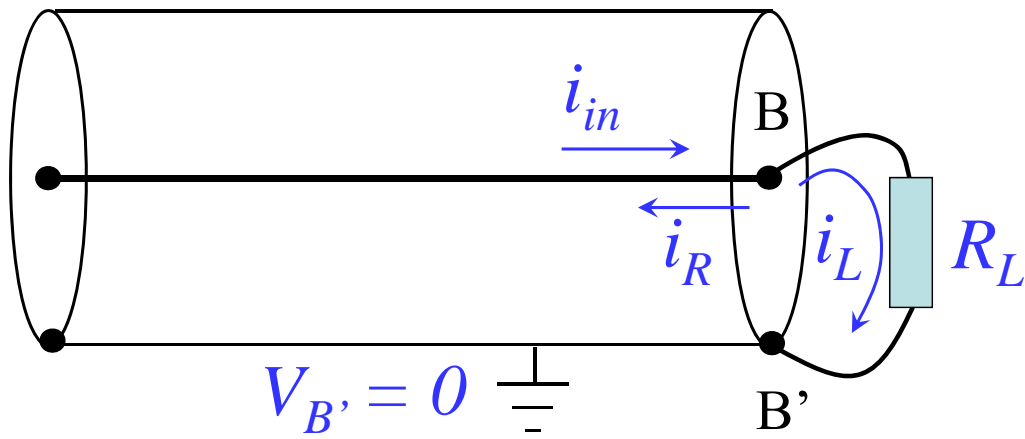


inside cable


outside cable

$$V_B = i_{in} Z_0 + i_R Z_0 \quad V_B = i_L R_L$$

not $V_B = i_{in} Z_0 - i_R Z_0$, *why?*

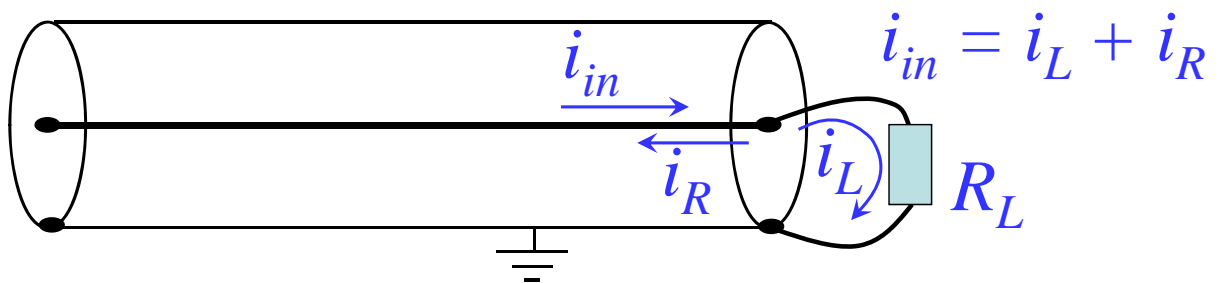

$$V_B = i_{in} Z_0 + i_R Z_0$$

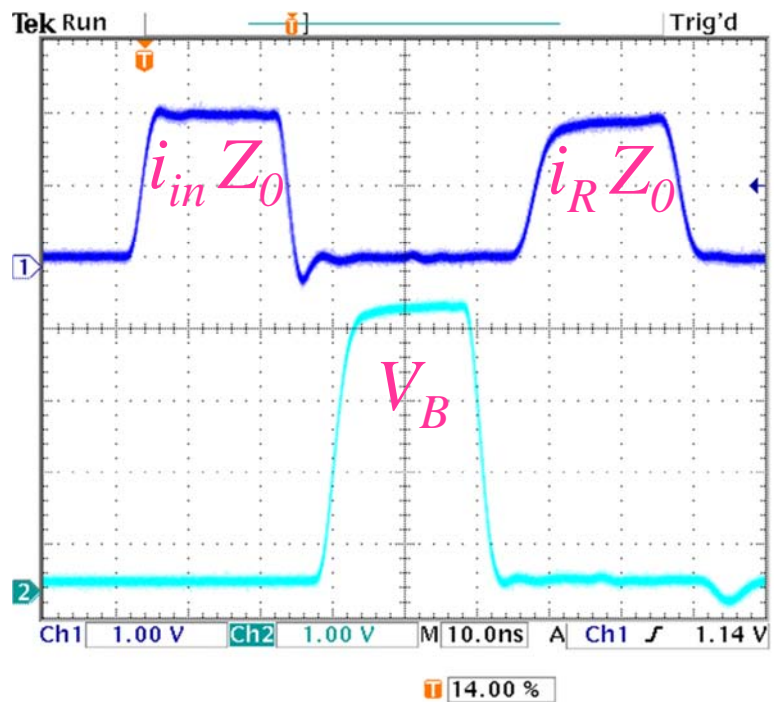

Load = short (0Ω)


$$V_B = i_{in} Z_0 + i_R Z_0 = 0$$

$$i_R = -i_{in}$$

$$i_L = i_{in} - i_R = 2 i_{in}$$

General solution:
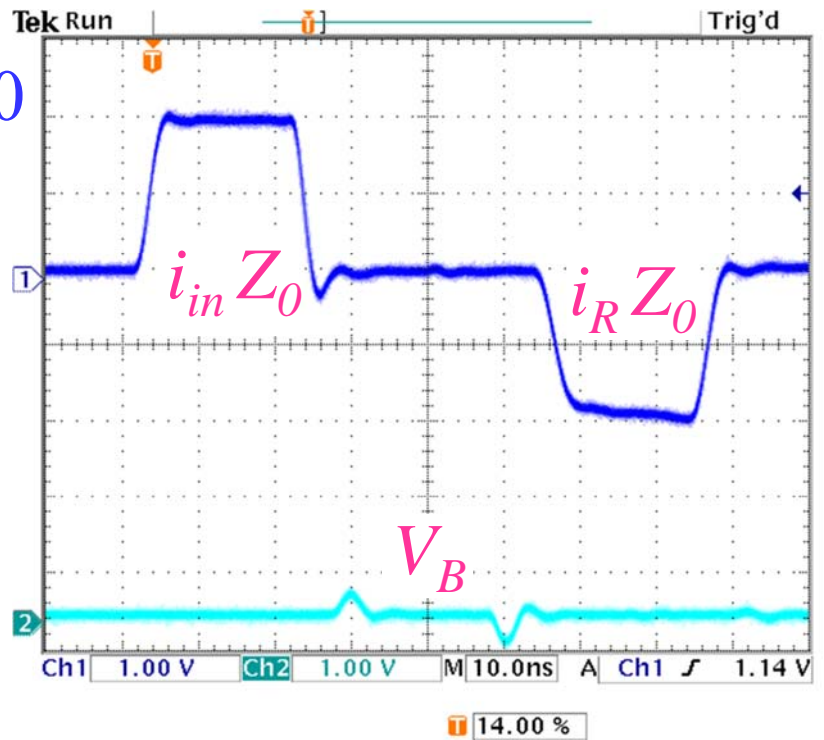
$$\Gamma = \frac{i_{in}}{i_R} = \frac{R - Z_0}{R + Z_0}$$



27

Doing this Simulated Research:

To measure something new (at least for the students)

To describe and explain the measurements

(記者 → 科學家)


To build a model (think, analysis, be creative)

To confirm every assumption of the model by experiments
(be careful)

To predict new things with the model
(knowledge becomes useful)


28

Load = 10 nF (capacitor)

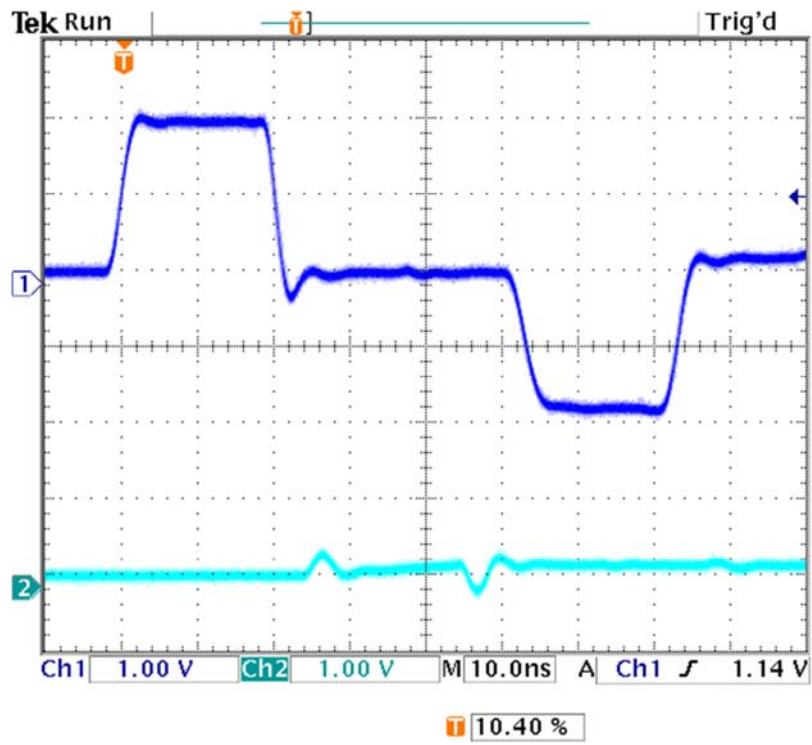

29


Load = 1 nF (capacitor)

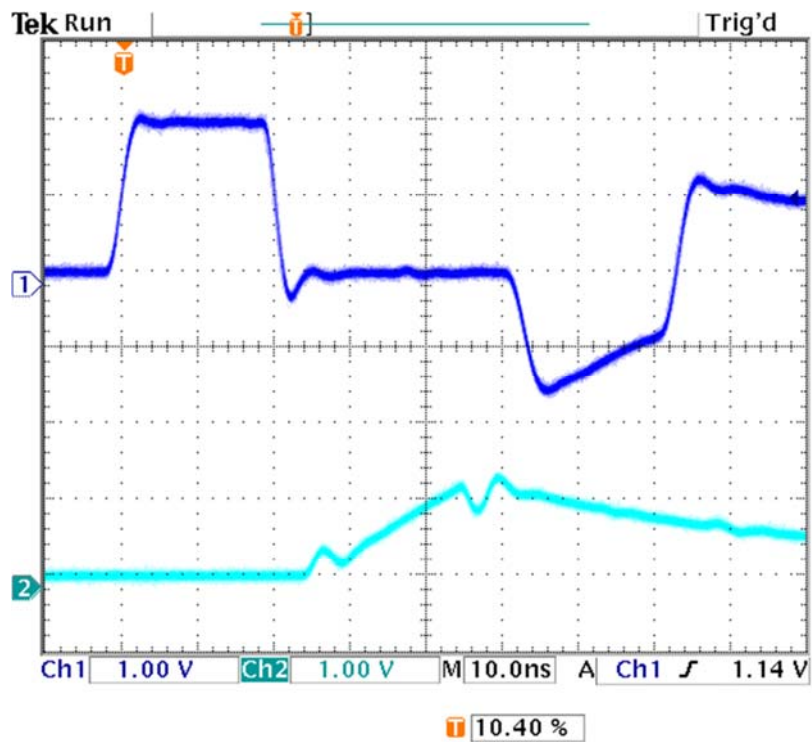

30


Load = 1 nF (capacitor)

At longer pulse width and time scale

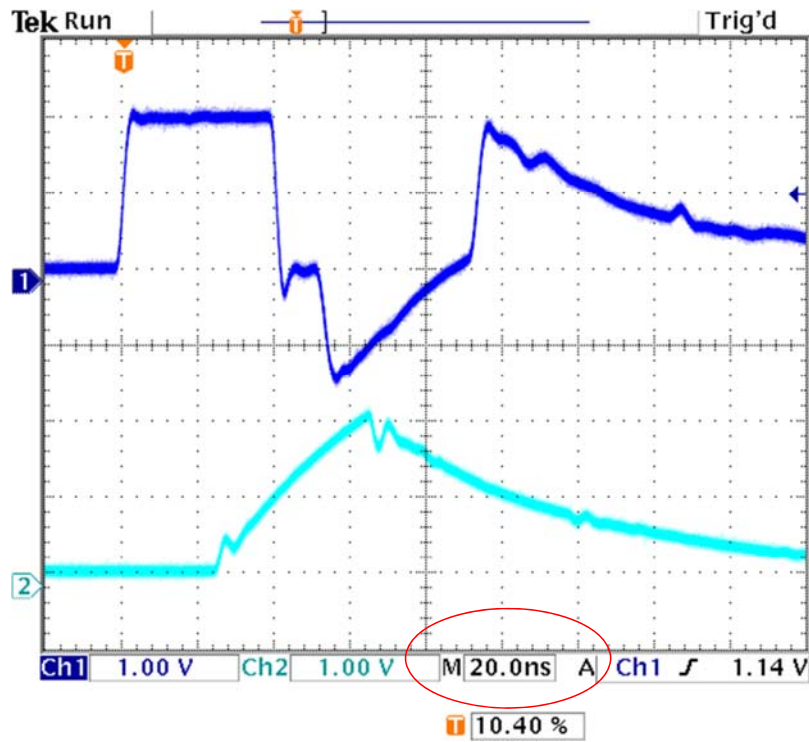


31

Load = an iron-core Coil (inductor)

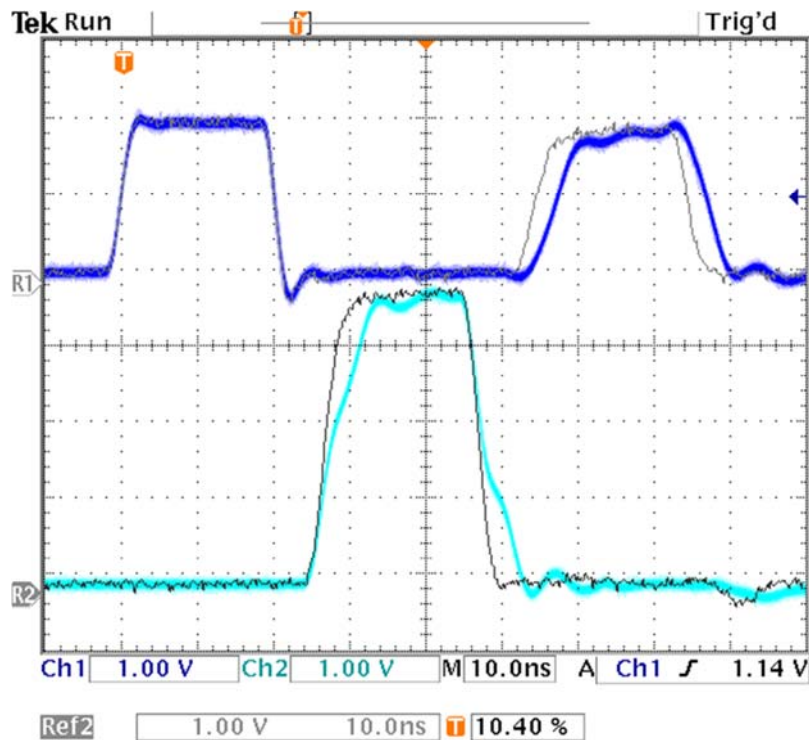


32

Load = an air-core Coil (inductor)

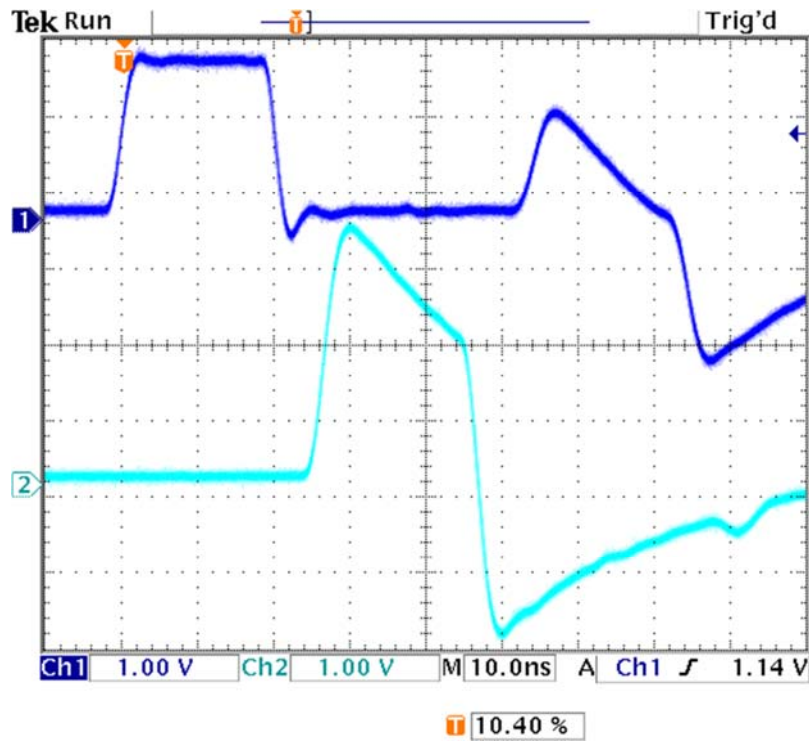

33

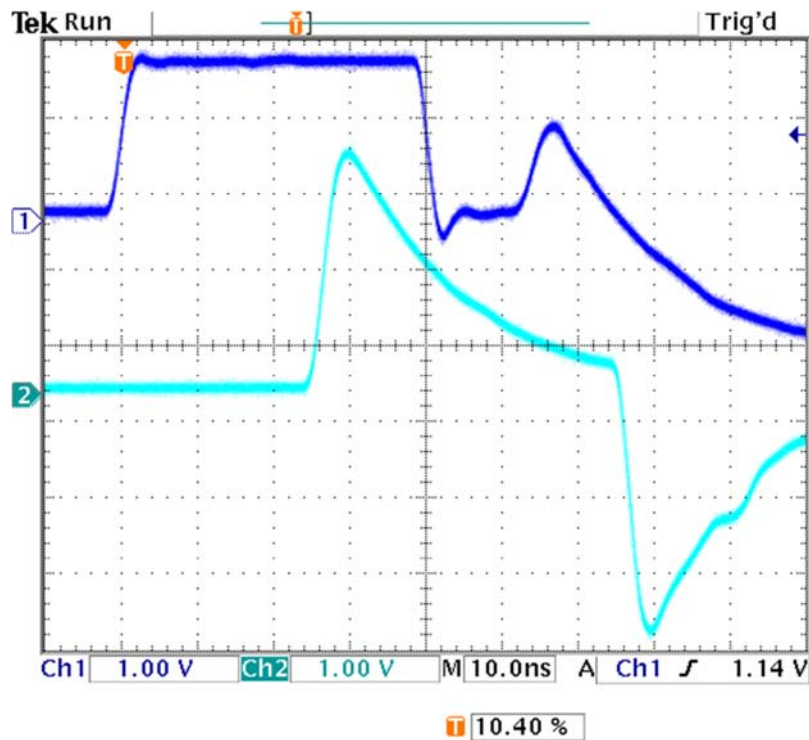
Load = a **Shorter** air-core Coil & **Longer** pulse width



34

Load = a **Shorter** air-core Coil & **Longer** pulse width

Shown at a longer time scale

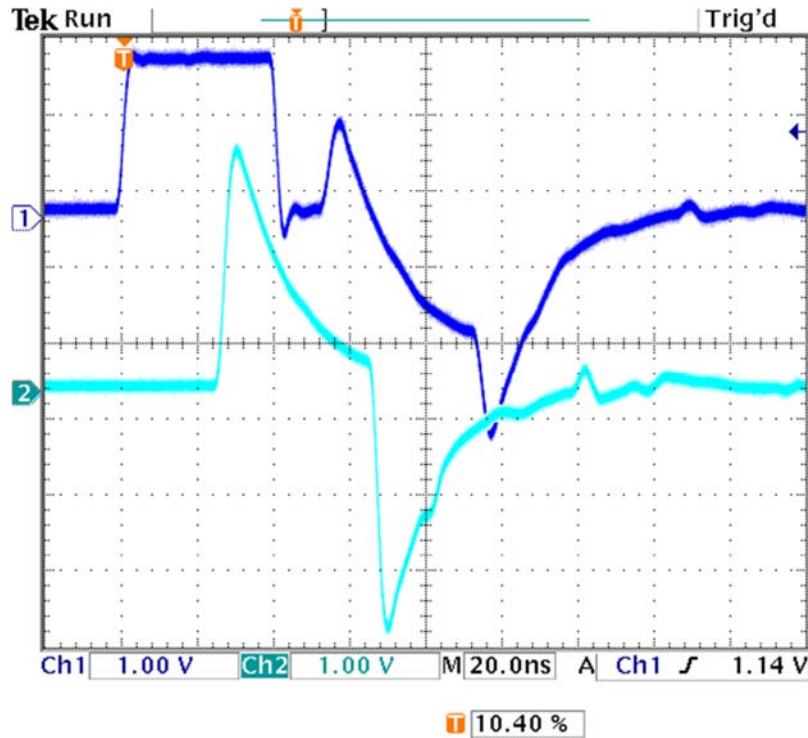


35

More Physical Concepts:

1. For a capacitor, its Voltage is a continuous function of time because Q is a continuous function of time.

$$Q = CV = \int i dt$$

$$i = \frac{dQ}{dt}$$

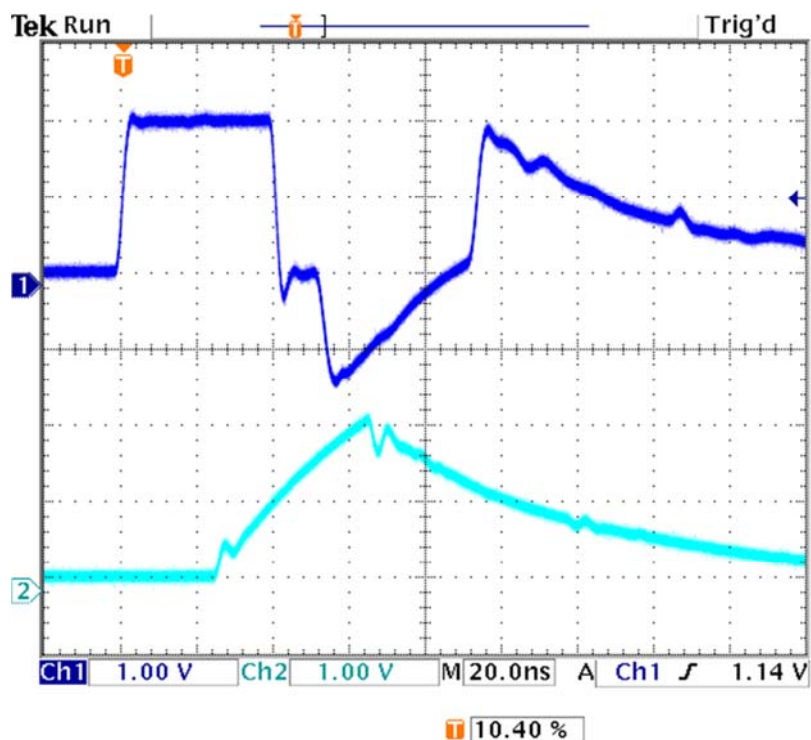


19 Aug 2012
18:30:50

36

More Physical Concepts:

2. For an Inductor, its Current i is a continuous function of time because V is finite.

$$V = L \frac{di}{dt}$$

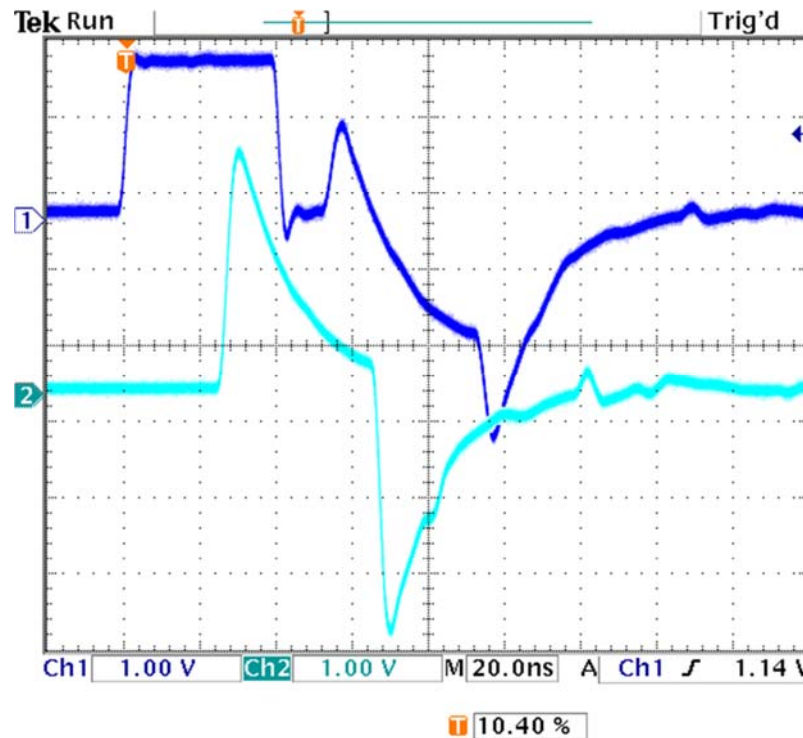

19 Aug 2012
18:20:37

37

More surprises in the experiments.

Interesting Observation #1:

For ≤ 100 students, from high school to postdoc,


Performance does not depend on previous level of education; **Knowing calculus helps a bit but is not enough.**

Persistence to think is important.

In average, the older, the worse.


39

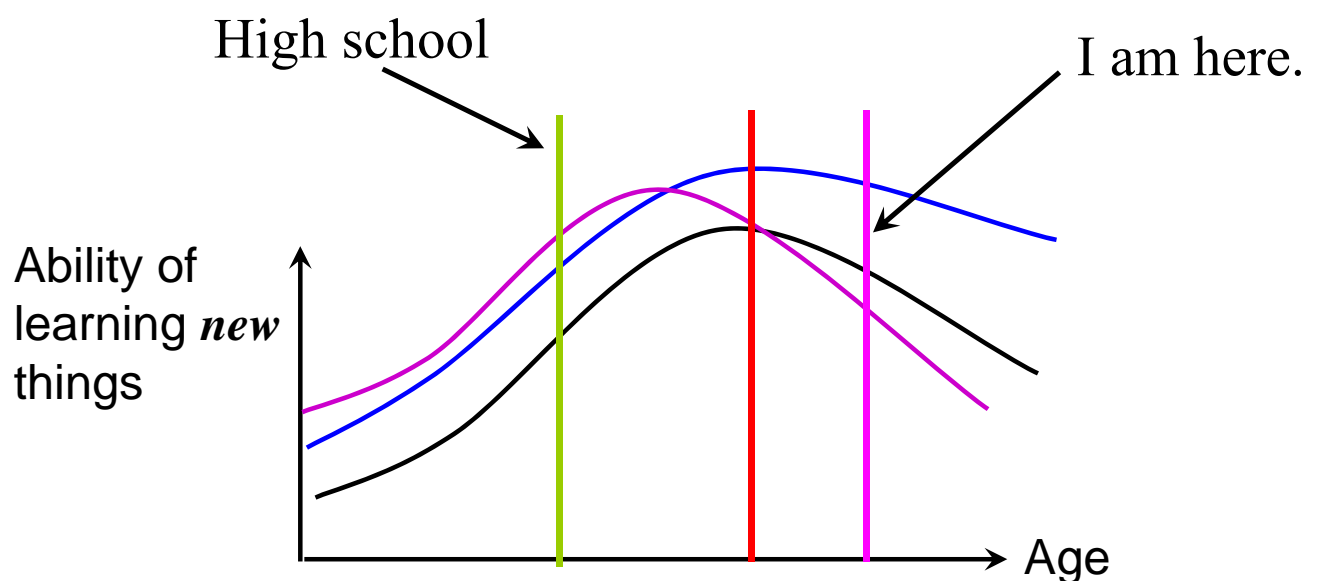**It is true that an old dog can't learn new tricks.
It may be different for *Homo sapiens*.**



by 林志民

40

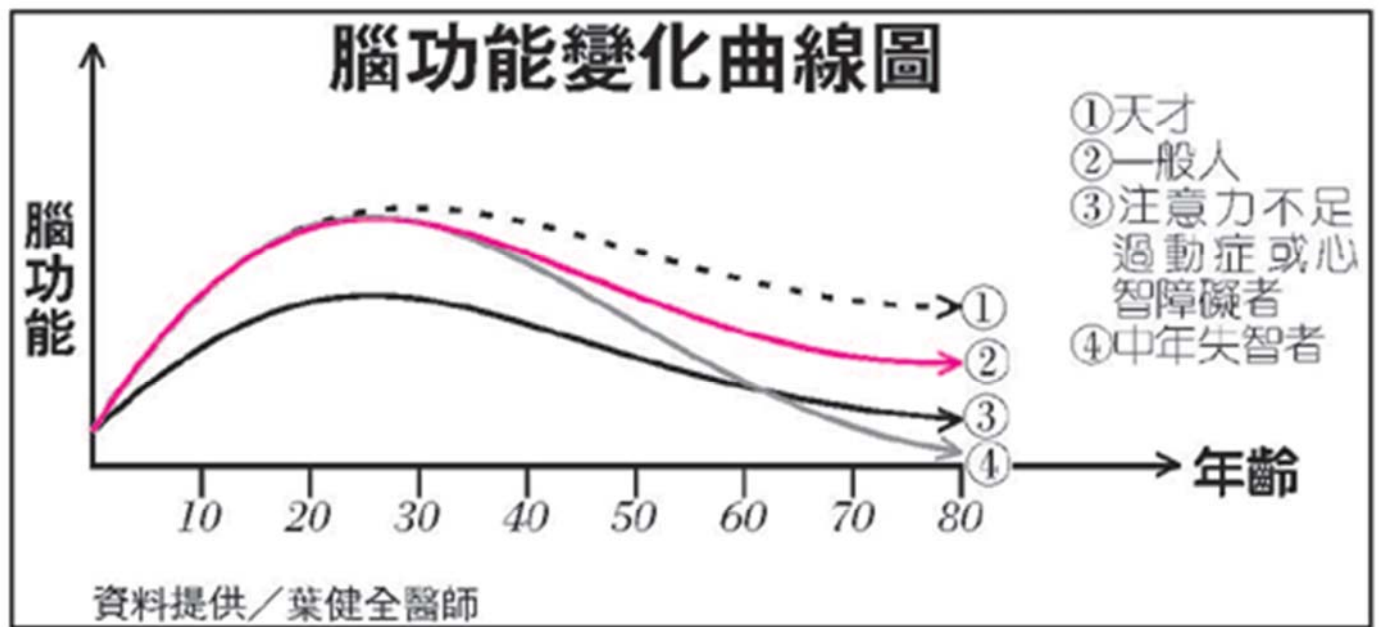

41

Interesting Observation #2:

≤ 100 students,

Some are very impressed, but some are not. Some of them forget after a while.

Some students who figured out the model by themselves appreciate this course very much.

42

Important aspects of doing experiments:

Separate meaningful physical quantities from those caused by imperfection of instruments and human operations. Thus, a model is useful.

To examine the assumptions of the model by experiments.

43

產生高電壓短脈衝方波的經濟方法

A New Economic Method to Generate Fast High Voltage Pulse

科儀新知第二十六卷第二期 93.10 65

鍾介文、林志民

Jieh-Wen Tsung, Jim Jr-Min Lin

利用電荷在傳輸線(此為同軸電纜)中等速傳輸的特性，將一定長度的同軸電纜充電至高壓後，再用快速電晶體開關瞬間將電荷導向與傳輸線匹配的負載，即可產生方波，其寬度由傳輸線的長度與訊號傳遞的速度來決定。此裝置可以輸出極高瞬間功率的脈衝，實測輸出至 50 Ω 負載之最高電壓達 1380 V，最短脈寬小於 20 ns。此法取材容易，造價低廉，產生脈衝的波形相當接近理想的方波，且穩定度極佳，具有不下於高價儀器的品質，應有很高的應用價值。

44


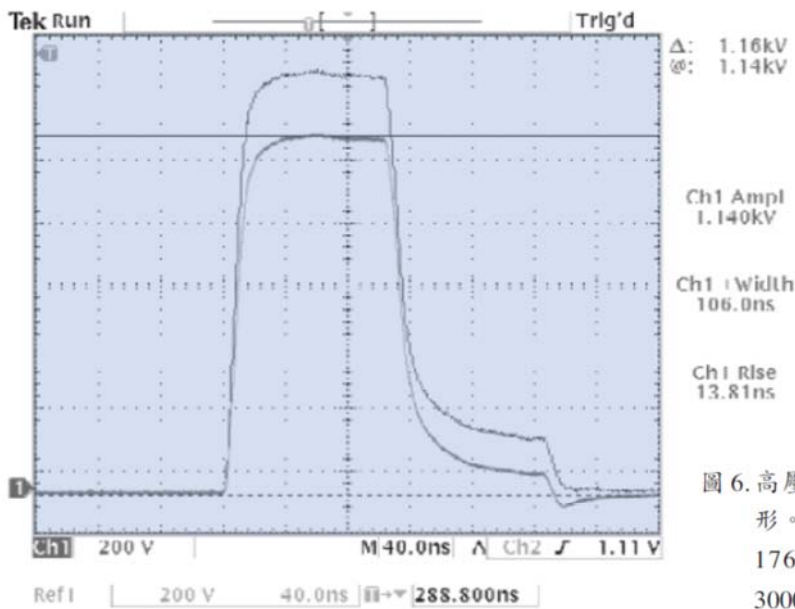


圖 6. 高壓短脈衝反射之波及其經過補償後的波形。Ref1 是未經過補償的波形，Ch1 是經過 176 Ω 阻補償後的波形。兩訊號之 V_0 皆為 3000 伏， C_d 長度為 11.579 公尺。

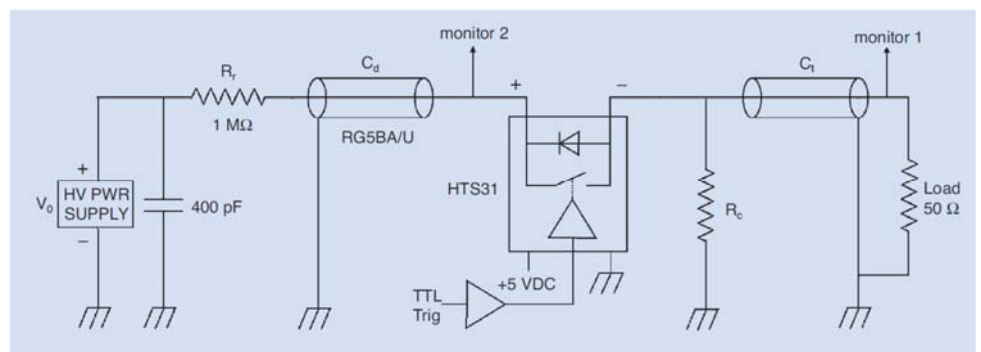

Important aspect of education:

Too easy is not interesting, but

too difficult is scaring.

Partial solution:

Provide necessary background knowledge (math).

*Thanks to
those students who spent a lot of time and
thought
on
these experiments.*