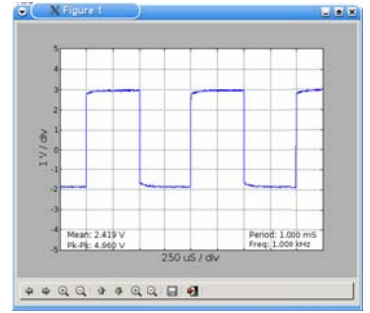


用電子訊號作工具來學科學

示波器：顯示電壓隨時間的變化(需要電流嗎? 輸入阻抗=?), 電子世界的眼睛





Trigger: Trigger Level, Trigger Slope and Trigger Mode (讓波形不跳動)

可測量：示波器內建參考方波、電池之電壓、交流電之波形(用衰減探棒)、雜訊、小馬達發電...

示波器問世之前, See 張文亮著 電學之父—法拉第的故事「第十五章電磁感應交響曲」
Google search: “第十五章電磁感應交響曲”


Remember the Ohm's law. It is useful all the time.

電容：Q = CV

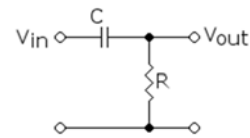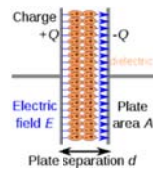



High pass filter: Image how it works.

想像一下它是如何運作的

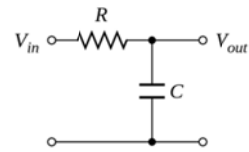

Low pass filter:

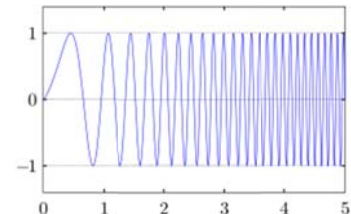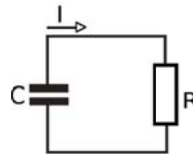With a chirped sinusoidal wave, we can see the frequency response.





RC circuit:

$$i = -dQ/dt = -CdV/dt$$

$$V = iR = -RCdV/dt \quad dV/dt \propto V$$

This is a first-order kinetic equation, which happens very often in research and in nature (almost everywhere).

See “指數函數及其斜率.docx”

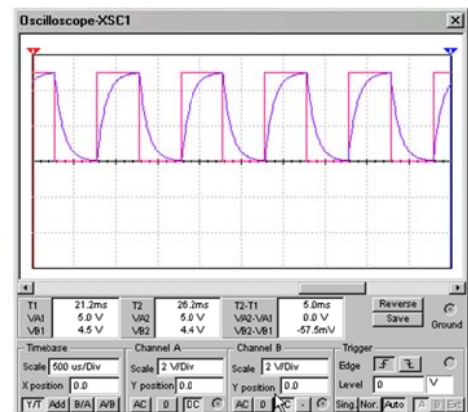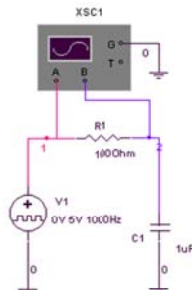


空電容 Vs. 充滿的電容 AC Vs. DC

⊕ 電感： $V = L di/dt$

To achieve a much higher voltage than the input voltage.

e.g., 點火線圈, ...

用電流來思考 (電流須連續?)

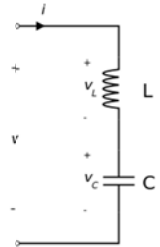

⊕ LC circuit:

$$V = V_C + V_L$$

Measure the peak-to-peak values of V , V_C and V_L at resonance and at off-resonance?

⊕ Complex Impedance is useful in analyzing L and C. See

<http://hyperphysics.phy-astr.gsu.edu/hbase/electric/impcom.html>


⊕ Euler's formula in complex analysis is very helpful.

$$e^{ix} = \cos(x) + i \sin(x) \quad i = \sqrt{-1}$$

for example: $e^{ix} e^{iy} = e^{i(x+y)}$ such that

$$[\cos(x) + i \sin(x)][\cos(y) + i \sin(y)] = \cos(x+y) + i \sin(x+y)$$

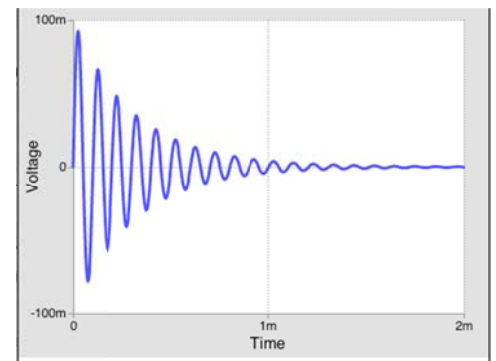See: https://en.wikipedia.org/wiki/Euler%27s_formula



⊕ 電波訊號傳遞與反射


When I was young, after sitting for 2 days in front of an oscilloscope, I understood how to imagine ...

Useful tips:

- (1) 電波之傳遞需要時間(接近光速?)
- (2) 電波在電纜中傳遞，當還沒到達末端時，
電波本身會覺得電纜是無限長的
- (3) 電荷不會憑空消失(Where the charges go?)
- (4) 電阻的運作遵守歐姆定律， $\Delta V = IR$ ，
 ΔV 為電阻兩端之電壓差

⊕ 物理模型與實驗相互修正...

答案是可以在示波器上看見的，學習如何看見

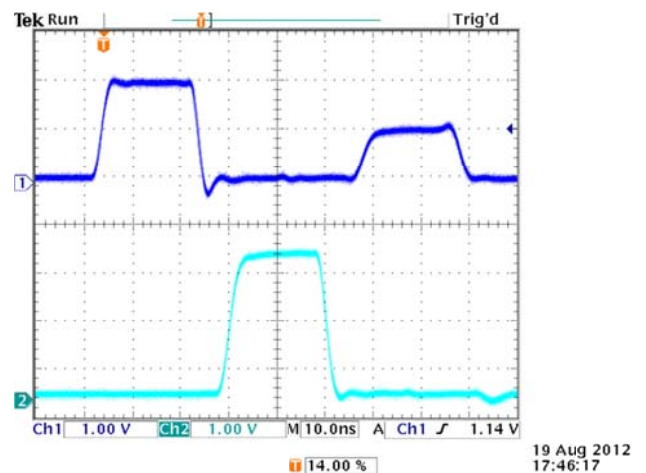

實驗觀察可暗示模型；好的模型可解釋實驗並能做預測

Picture source: Wiki